


# Low-Level Digital Components

## Flip-Flop

- Has two stable states
- Can store information
- Also called a "Latch"

## Full-Adder


- Adds binary numbers and the carry

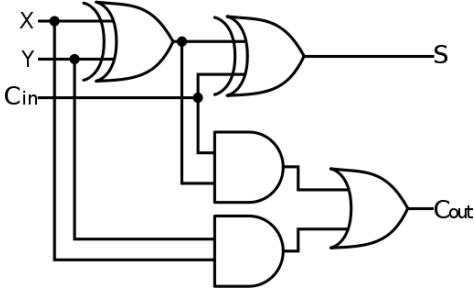

Inputs			Outputs	
X	Y	C <sub>in</sub>	C <sub>out</sub>	S
0	0	0	0	0
1	0	0	0	1
0	1	0	0	1
1	1	0	1	0
0	0	1	0	1
1	0	1	1	0
0	1	1	1	0
1	1	1	1	1
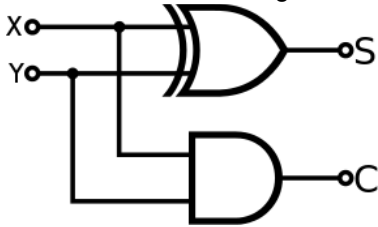
## Half-Adder


- Adds two single-digit binary numbers
- Outputs the sum and carry
- Uses an XOR and AND gate



Inputs			Outputs
X	Y	C	S
0	0	0	0
1	0	0	1
0	1	0	1
1	1	1	0

## JK Latch


- An SR Latch designed to toggle

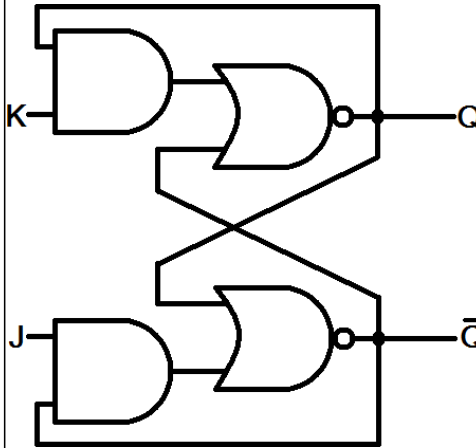

J	K	Result
0	0	No Change
0	1	Reset
1	0	Set
1	1	Toggle

## SR NAND Latch

- Made with two NAND gates

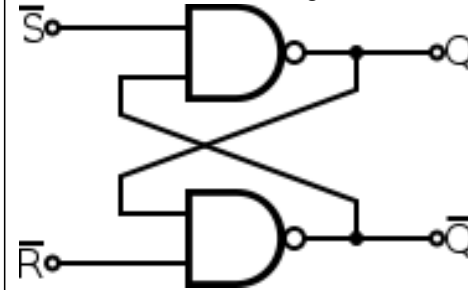

S̄	R̄	Result
0	0	Not Permitted
0	1	Q=1
1	0	Q=0
1	1	Not Permitted

## SR NOR Latch

- Most fundamental latch
- Made with two NOR gates

